

Name: Gaurav Pant Student ID: 21711019

①

Enrollment no: PR-21010071 Course: MCA 1A

Semester: 1 Sem Paper Name: Computer Organization and Architecture Lab

University Roll no.: 2101071

### Q1) NAND Gate

Apparatus Required: NAND gate IC, power supply, Hook up wires and breadboard etc.

Theory (Working): NAND gate is actually series of AND gate with NOT gate. If we connect the output of an AND gate to the input of a NOT gate, this combination will work as NOT-AND or NAND gate.

- Its output is 1 when any or all inputs are 0, otherwise output is 0.
- The logic NAND gate is generally called as a "UNIVERSAL GATE" because it is one of the most used logic gate types.

Gant



Procedure:

- \* Connect the VCC and ~~g~~ ground to the pins specified by the data sheet.
- \* Do all the connections as per the IC diagram, switch on the power supply
- \* After completing the connections, properly observe the output and match it with the given truth table.

~~Result: The result of the experiment has been verified successfully~~

Truth Table


Input		Output
A	B	$C = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

Name: Gaurav Pant

Student ID: 21711019

②


### IC Diagram

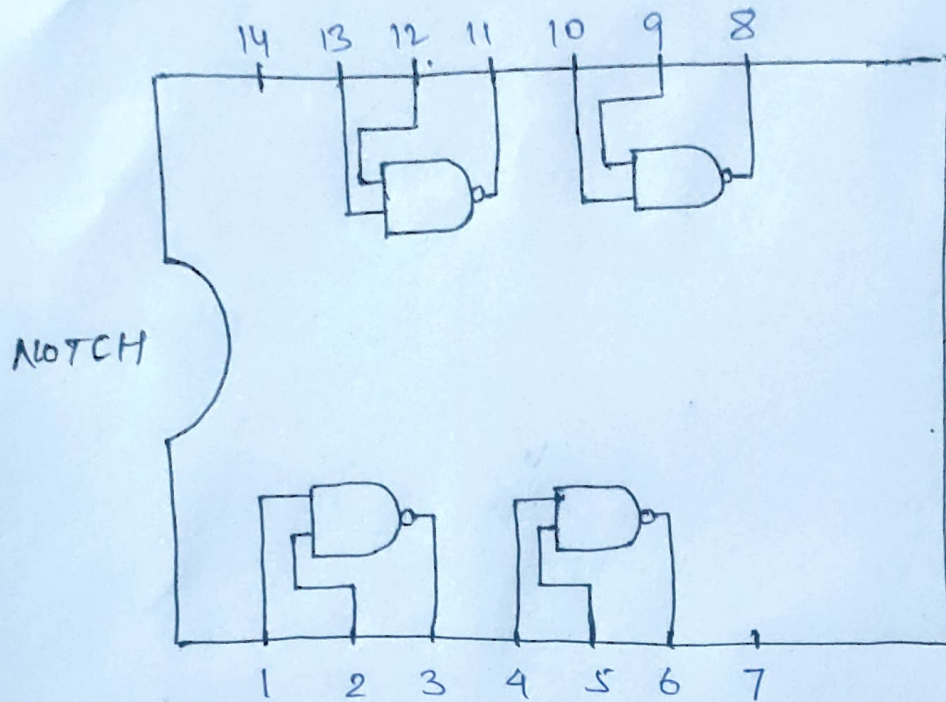

NOTCH

IC-7400

### Logic Diagram

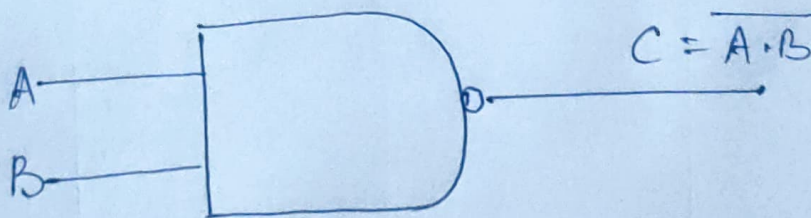

Gaurav