

Name → Manish Singh

Page 1

University Roll No → 2101106

Course → MCA I B

Practical Name → Computer Organization mid-term


Practical Code → PMC 102

Date → 22/03/2022

Q1 ⇒ Discuss the working of NAND gate with the help of circuit diagram and truth table.

Theory ⇒ The NAND gate is a combination of an AND gate and NOT gate. They are connected in cascade form. It is also called Negated AND Gate. The NAND GATE provides the false or low output only when their outputs is high or true.

IC-Diagram ⇒

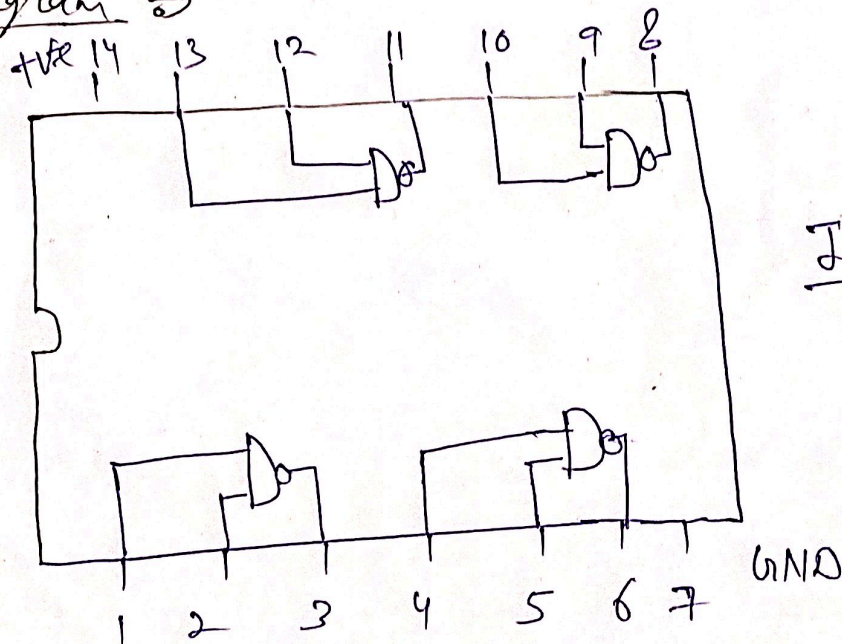


IC No. 7400

~~Manish Singh~~

Circuit Diagram \Rightarrow

Page 2

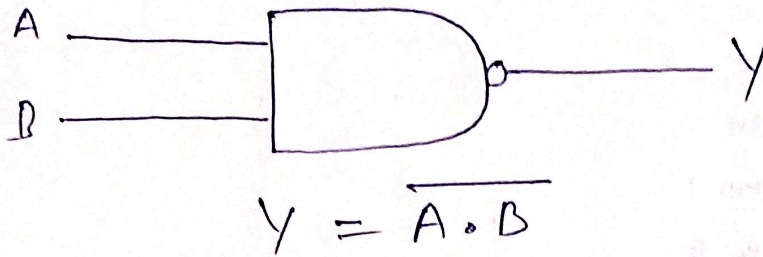

Truth Table \Rightarrow

A	B	$Y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

NAND gate is a NOT gate followed by an AND gate, so if we can cancel the effect of NOT gate in a NAND gate, it will become an AND gate. Hence, a NOT gate followed by a NAND gate realize an AND gate.

\Rightarrow From the truth table of the gate, it is clear that all the inputs must be high to get a low output and if any of the input is low, the output obtained will be high. If any one of the input is also high the output will be high that is 1.

My Singh